

# Solar Collector



# Control System/Electronics



# Tank



# Thermal-Circuit Equivalents

Heat [K] = Voltage [V]  
Power [W] = Current [I] = Coulombs/Sec [Q/s]

## Electrical:

$$C = [Q/V]$$

$$R = [V/I] = [V \cdot s/Q]$$

$$L = [V \cdot s/A] = [V \cdot s^2/Q]$$



## Thermal:

$$C = [J/K]$$

$$R = [K/W] = [K \cdot s/J]$$

$$L = [K \cdot s/W] = [K \cdot s^2/J]$$

# Feed Forward System

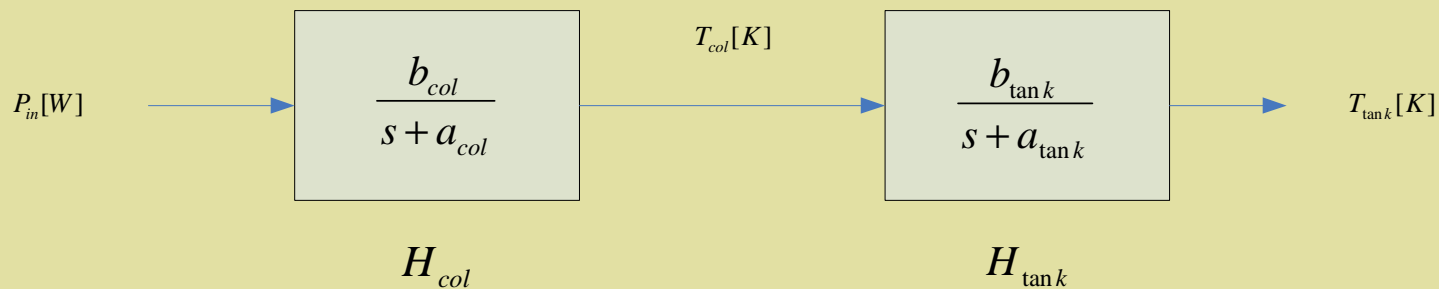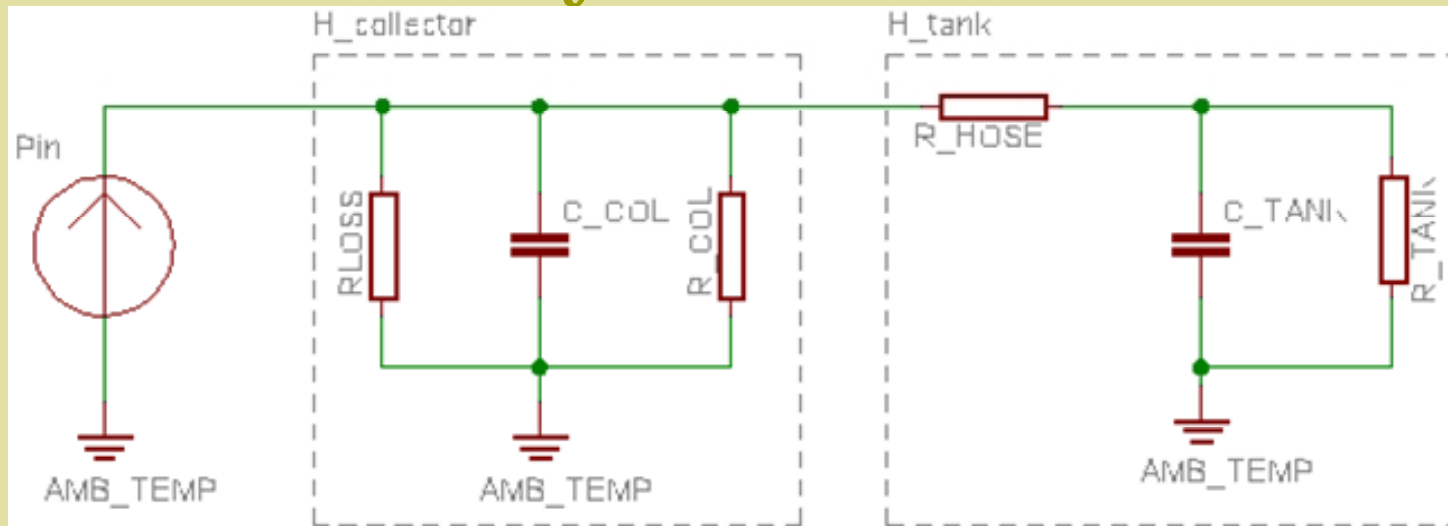

$$a_{col} = \frac{R_{loss} + R_{col}}{C_{col} R_{loss} R_{col}}$$


$$a_{tank} = \frac{R_{hose} + R_{tank}}{C_{tank} R_{hose} R_{tank}}$$

$$b_{col} = \frac{1}{C_{col}}$$


$$b_{tank} = \frac{1}{C_{tank} R_{hose}}$$




# Sensors

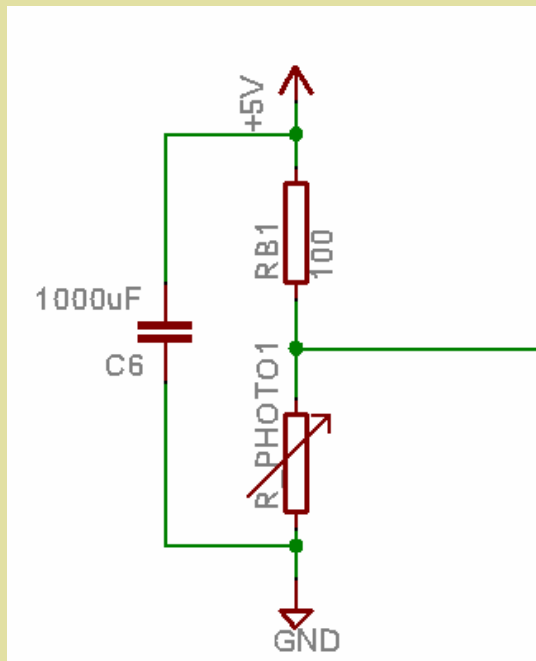

Light Sensor

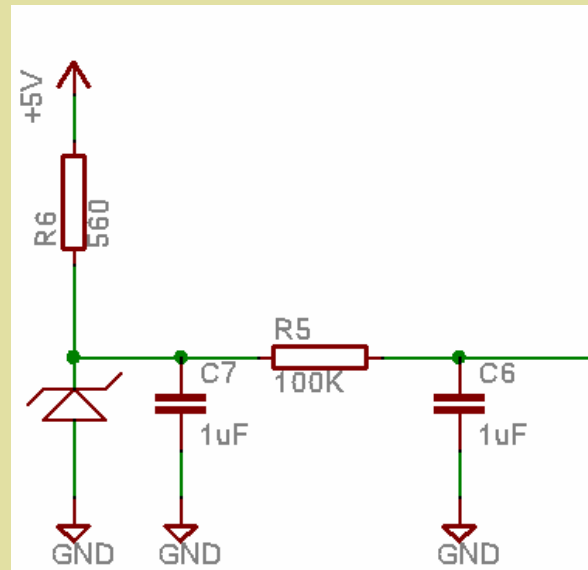


Temperature Sensor

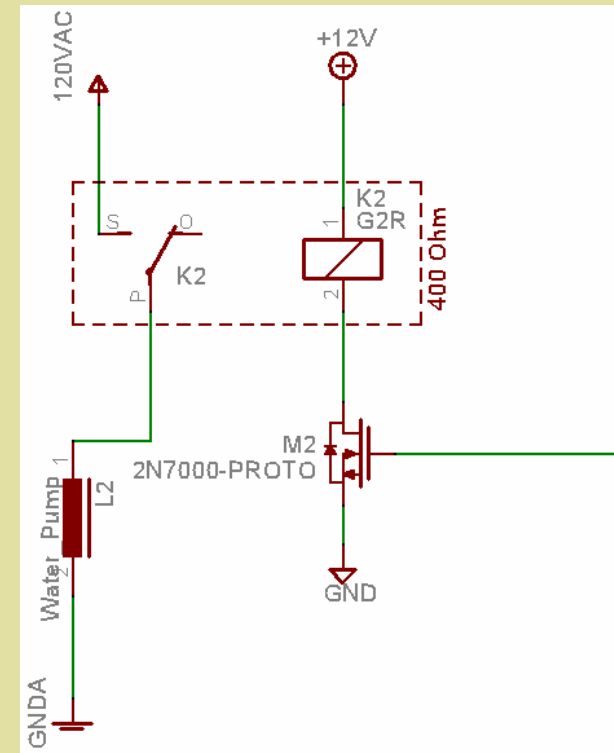


Power Relay

# Light Sensor


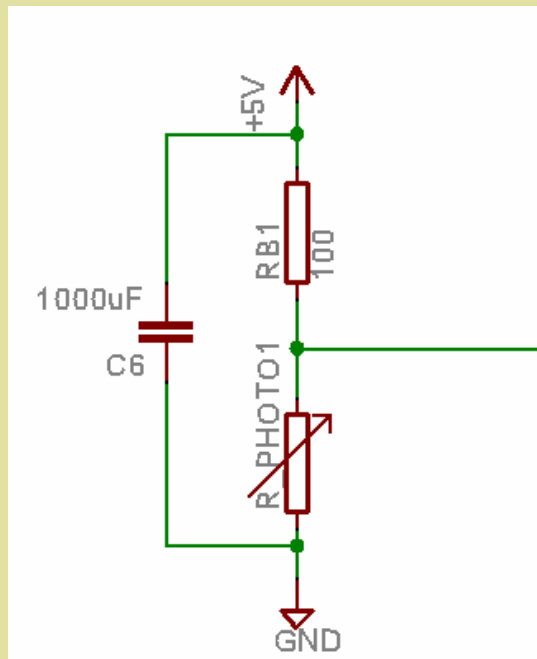


Light Sensor

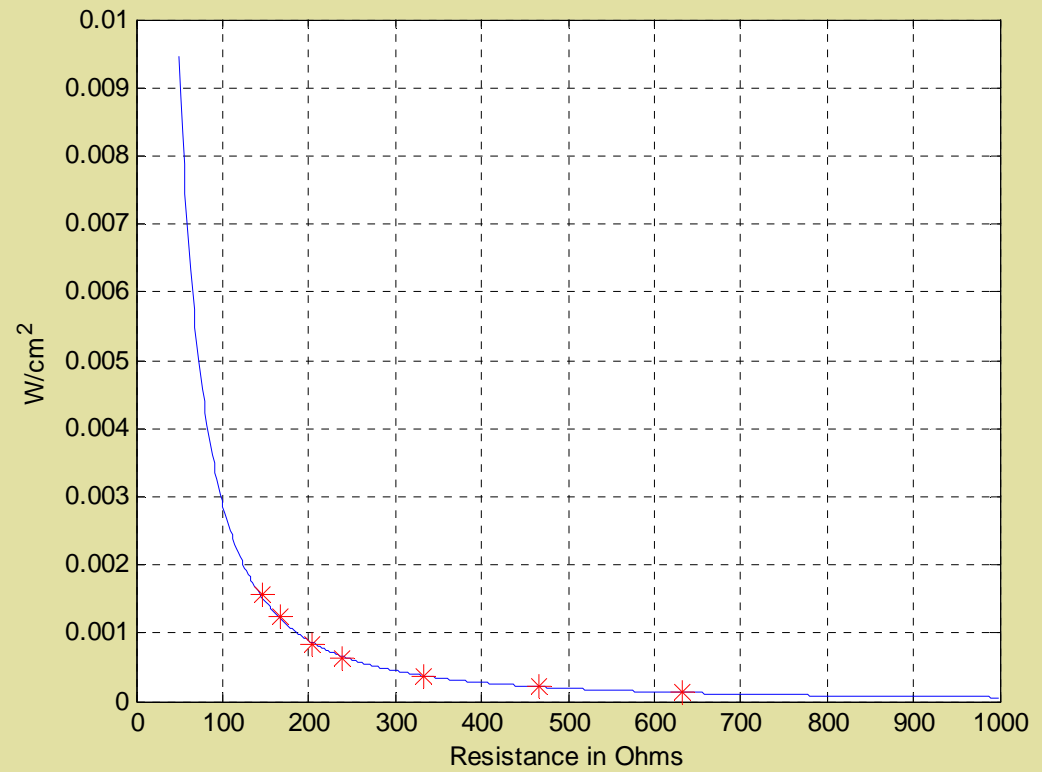

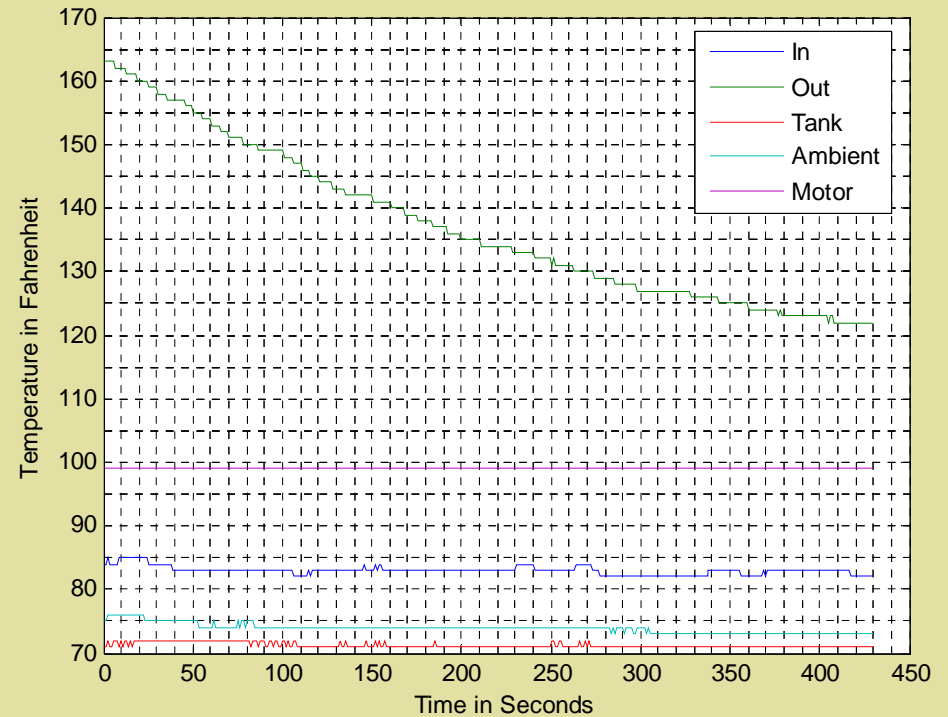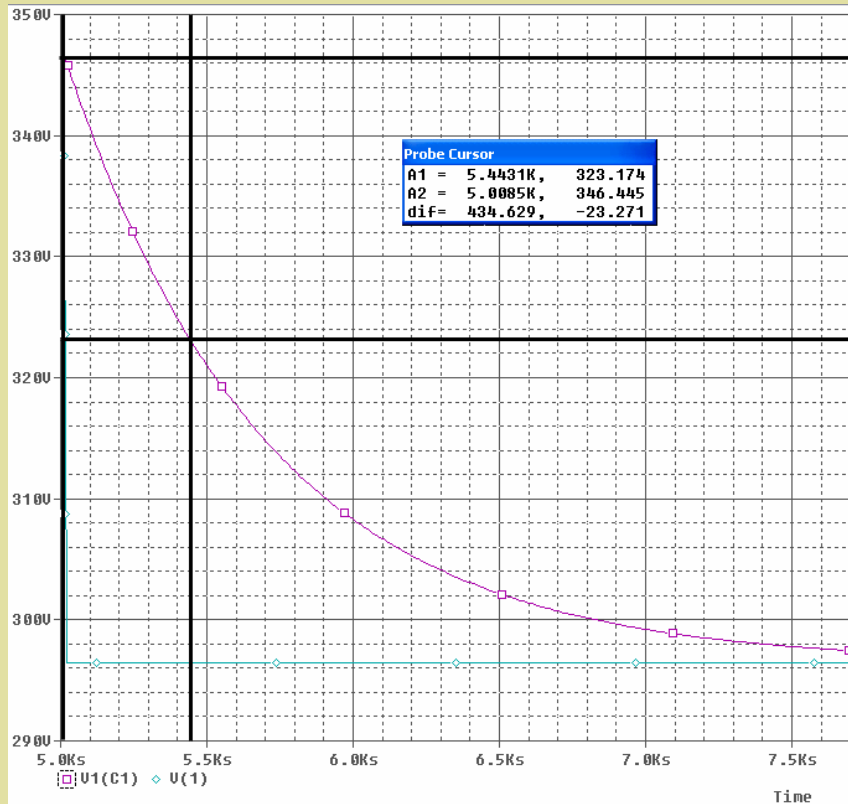
# Finding Component Values: Rcol

$$V_c = V_{t=0} * e^{\frac{-t}{RC}} \quad \Leftrightarrow \quad R = \frac{-t}{C * \ln(\frac{V_c}{V_{t=0}})}$$






# Feed Back System

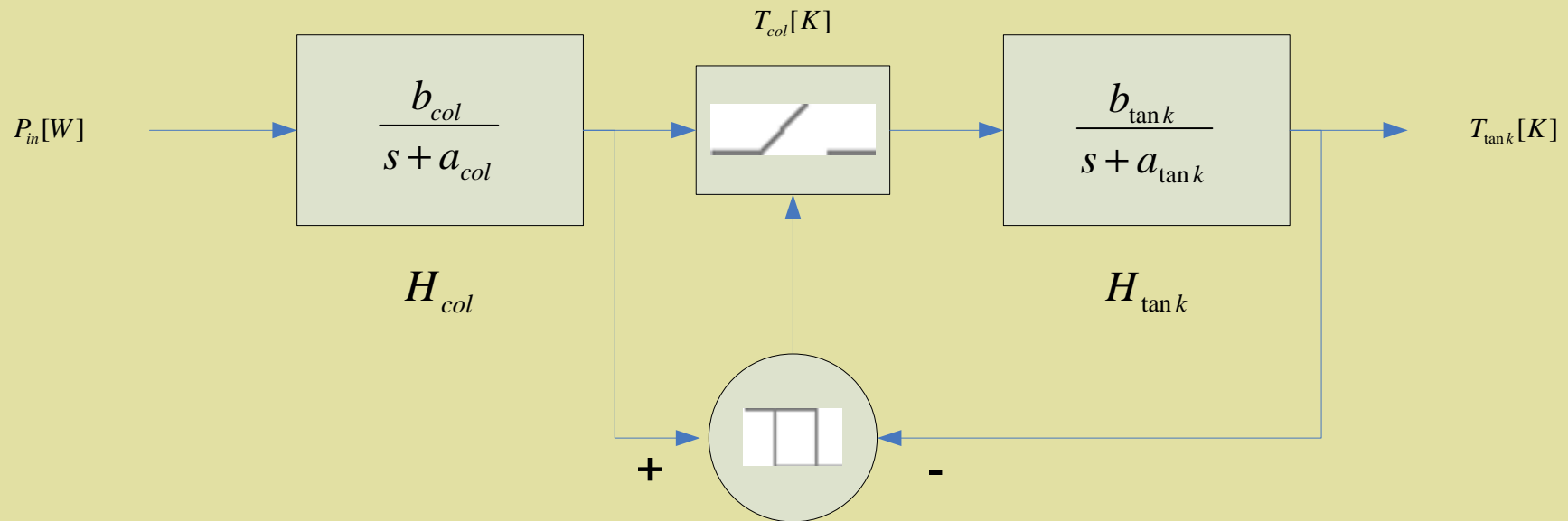

# Model Comparison

Measured Results

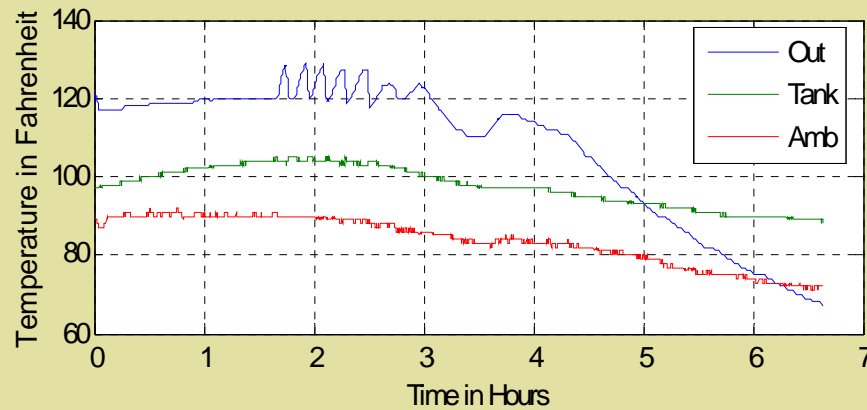

Simulation Results

